

Analysis of the Tuggle Front End

This article analyzes the Tuggle tuner, of common use in high-performance DX crystal sets. An equivalent circuit for the antenna-ground system with the tuner connected is shown in Fig. 1 below. It must be recognized that there is some stray capacitance of the rotor and frame of the two-gang variable capacitor to ground. This should be shown as a fixed capacitor across the bottom variable capacitor. Its presence will reduce the maximum frequency to which the circuit will tune. However, in the present analysis this stray capacitance is neglected.

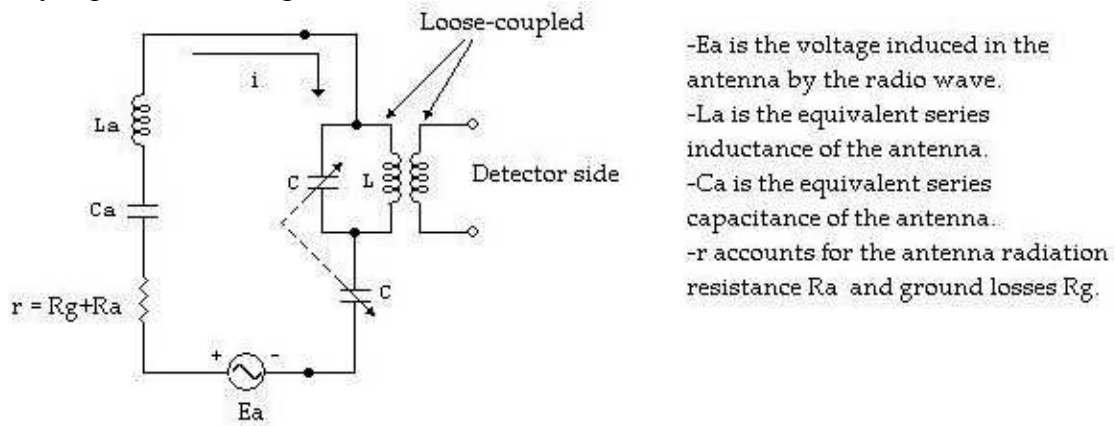


Fig. 1 The Tuggle front end connected to an antenna-ground system

The mesh current is described by:

$$I = \frac{Ea}{r + j\left(\omega La - \frac{1}{\omega Ca}\right) + \bar{Z} - \frac{j}{\omega C}} \quad \dots(1)$$

$$\bar{Z} = \frac{1}{\bar{Y}}$$

where:

$$\begin{aligned} \bar{Y} &= \frac{1}{j\omega L} + j\omega C \\ &= j\left(\omega C - \frac{1}{\omega L}\right) \\ &= j\left(\frac{\omega^2 LC - 1}{\omega L}\right) \end{aligned}$$

$$\therefore \bar{Z} = \frac{1}{j\left(\frac{\omega L}{\omega^2 LC - 1}\right)}$$

or:

$$\bar{Z} = j \left(\frac{\omega L}{1 - \omega^2 LC} \right)$$

Then, $I = I_{MAX}$ when:

$$\left(\omega La - \frac{1}{\omega Ca} \right) + \left(\frac{\omega L}{1 - \omega^2 LC} \right) - \frac{1}{\omega C} = 0$$

This is, when:

$$\omega \left(La + \frac{L}{1 - \omega^2 LC} \right) - \frac{1}{\omega \left(\frac{CaC}{Ca + C} \right)} = 0 \quad \dots(2)$$

which is satisfied at certain radian frequency ω_r .

At this frequency, the L-C tank circuit behaves as an equivalent inductance

$$\frac{L}{1 - \omega_r^2 LC}$$

Usually, L is much greater than L_a for antennas used in crystal set work. Then,

$$La \ll \frac{L}{1 - \omega_r^2 LC}$$

Equation (2) can be written as:

$$\frac{\omega_r L}{1 - \omega_r^2 LC} - \frac{1}{\omega_r \left(\frac{CaC}{Ca + C} \right)} = 0$$

We can then write:

$$\frac{\omega_r L}{1 - \omega_r^2 LC} = \frac{Ca + C}{\omega_r CaC}$$

After some algebraic manipulation we obtain:

$$\omega_r^2 LC \left(\frac{2Ca + C}{Ca + C} \right) = 1 \quad \dots(3)$$

The equivalent capacitance resonating with L is:

$$C_{eq} = C \left(\frac{2Ca + C}{Ca + C} \right)$$

Clearly, $C_{eq} > C$.

Following is a numerical example illustrating the use of the above results.

Let C be a variable capacitance with $C_{MIN} = 20$ pF and $C_{MAX} = 475$ pF. Let also C_a be 200 pF. Then, C_{eq} varies between $C_{eqMIN} = 38.18$ pF and $C_{eqMAX} = 615.74$ pF.

If we wish to tune the MW broadcast band starting at 530 kHz, then the required inductance L will be:

$$L = \frac{1}{\omega_{rMIN}^2 C_{eqMAX}}$$
$$= 146.45 \mu H$$

The circuit will tune up to:

$$f_{MAX} = f_{MIN} \left(\frac{C_{eqMAX}}{C_{eqMIN}} \right)^{\frac{1}{2}}$$
$$= 2.128 MHz$$

If we use for C a variable capacitance with $C_{MIN} = 20$ pF and $C_{MAX} = 365$ pF, then $C_{eqMIN} = 38.18$ pF and $C_{eqMAX} = 494.20$ pF, giving for the required inductance L a value of 182.46 μH . The circuit will tune up to $f_{MAX} = 1.906$ MHz.

Acknowledgements: Special thanks are given to Ben Tongue for his comments on the manuscript and for encouraging further mathematical analysis of the circuit regarding bandwidth variation with frequency, which will be done shortly.

Ramon Vargas Patron
rvargas@inictel.gob.pe
Lima-Peru, South America
March 14th, 2004

